

D: 14/11/20

North East University Bangladesh

Department of CSE

Assignment - 1


Program : B. Sc. (Engg.) in CSE

Course : CSE 121 (Basic Electrical Engineering)

Name : Ahmed All-kahir

Reg : 170103020038

Answer to the question no: 01

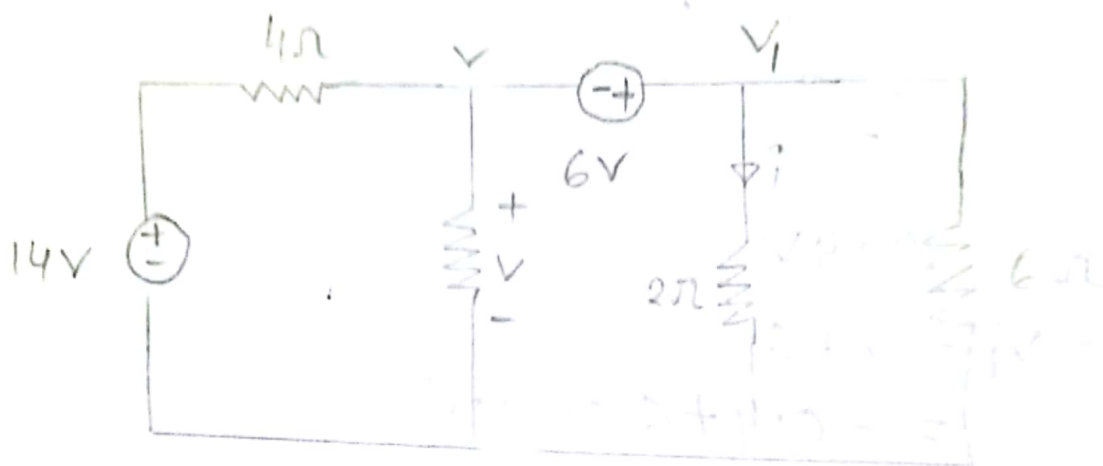

Solution: Super node, apply KCL

$$\frac{14-v}{4} = \frac{v}{3} + \frac{v_1}{2} + \frac{v_1}{6}$$

$$\Rightarrow \frac{14-v}{4} = \frac{2v+3v_1+v_1}{6}$$

$$\Rightarrow 84-6v = (2v+4v_1)4$$

$$\Rightarrow 84-6v = 8v+16v_1$$

$$\Rightarrow 84 = 14v + 16v_1 \text{ — (i)}$$

Apply KVL \rightarrow

$$-v-6+v_1=0$$

$$\Rightarrow v_1 = v+6 \text{ — (2)}$$

(1) no \rightarrow

$$84 = 14v + 16 \times (v+6)$$

$$= 14v + 16v + 96$$

$$= 30v + 96$$

P.T.O

$$\Rightarrow 84 - 96 = 30V$$

$$\Rightarrow -12 = 30V$$

$$V = \frac{-12}{30}$$

$$= -0.4V$$

$$\therefore V_1 = V + 6$$


$$= -0.4 + 6 = 5.6$$

$$\therefore i = \frac{V_1}{2} = \frac{5.6}{2} = 2.8A$$

$$\text{Ans: } V = -0.4V, V_1 = 5.6V$$

$$i = 2.8A$$

Answer to the question no: 2

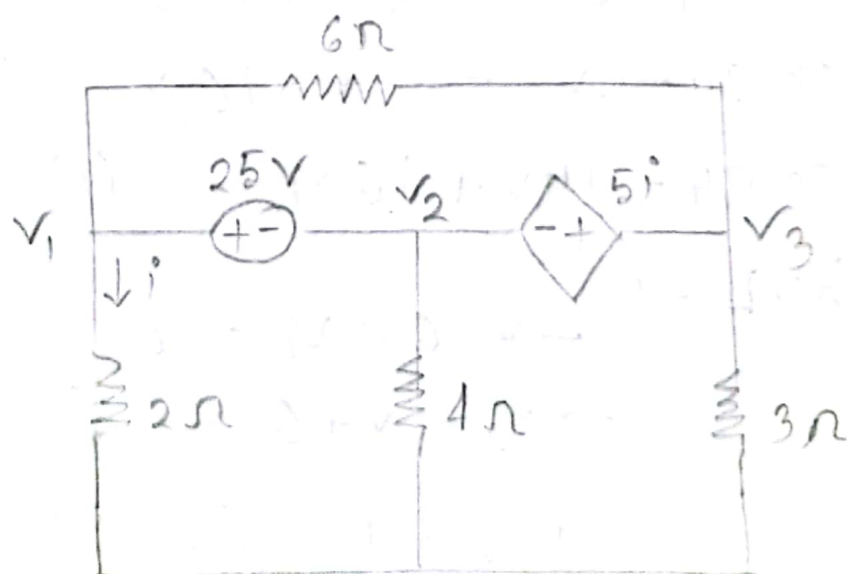

Solution: Apply KCL in both supernode

$$\frac{V_1}{2} + \frac{V_1 - V_3}{6} + \frac{V_2}{4} + \frac{V_3 - V_1}{6} + \frac{V_3}{3} = 0$$

$$\Rightarrow \frac{V_1}{2} + \frac{V_1}{6} - \frac{V_3}{6} + \frac{V_2}{4} + \frac{V_3}{6} - \frac{V_1}{6} + \frac{V_3}{3} = 0$$

$$\Rightarrow \frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{3} = 0$$

$$\Rightarrow \frac{6V_1 + 3V_2 + 4V_3}{12} = 0$$

$$\Rightarrow 6V_1 + 3V_2 + 4V_3 = 0 \text{ ——— (1)}$$

Apply KVL \rightarrow

$$-V_1 + 25 - V_2 = 0$$

$$\Rightarrow V_1 + V_2 = 25 \text{ ——— (2)}$$

$$-V_2 - 5i + V_3 = 0$$

$$\Rightarrow -V_2 + V_3 = 5i$$

$$\Rightarrow -V_2 + V_3 = 5 \times \frac{V_1}{2} \cdot \left[i = \frac{V_1}{2} \right]$$

$$\Rightarrow 2V_3 - 2V_2 = 5V_1$$

$$\Rightarrow 5V_1 - 2V_2 + 2V_3 = 0 \text{ ——— (3)}$$

using Cramer's rule,

$$\begin{bmatrix} 6 & 3 & 4 \\ 1 & 1 & 0 \\ 5 & -2 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 25 \\ 0 \end{bmatrix}$$

$$V_1 = 15.909V$$

$$V_2 = 9.09V$$


$$V_3 = -30.68V$$

$$\text{Ans: } V_1 = 15.909V$$

$$V_2 = 9.09V$$

$$V_3 = -30.68V$$

Ans. to the Q. NO : 03

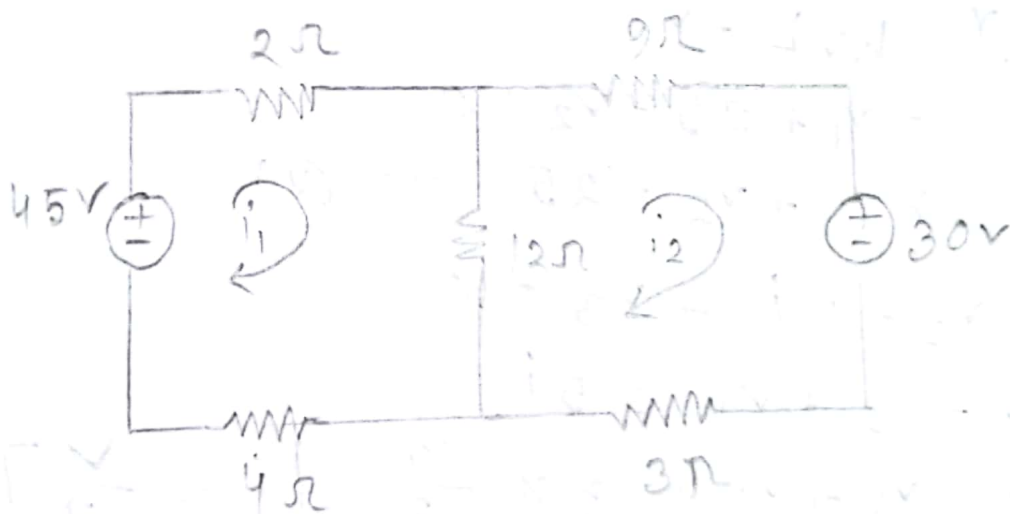

Solution: Apply KVL to Mesh-1:

$$-45 + 18i_1 - 12i_2 = 0$$

$$\Rightarrow -15 + 6i_1 - 4i_2 = 0$$

$$\Rightarrow 6i_1 - 4i_2 = 15 \quad \text{--- (i)}$$

in Mesh-2: $30 + 24i_2 - 12i_1 = 0$

$$\Rightarrow -2i_1 + 4i_2 = -5 \quad (2)$$

$$(1) + (2) \rightarrow 6i_1 - 2i_1 = 10$$

$$\Rightarrow 4i_1 = 10$$

$$\Rightarrow i_1 = \frac{10}{4} = \frac{5}{2} = 2.5 \text{ A}$$

$$= 2500 \text{ mA}$$

$$\therefore i_1 = 2500 \text{ mA}$$

$$6i_1 - 4i_2 = 15$$

$$\Rightarrow 6 \times (2.5) - 4i_2 = 15$$

$$\Rightarrow -4i_2 + 15 = 15$$


$$\Rightarrow -4i_2 = 0$$

$$\therefore i_2 = 0$$

$$\text{Ans: } i_1 = 2500 \text{ mA}$$

$$i_2 = 0 \text{ A}$$

Ans. to the Q. No : 04

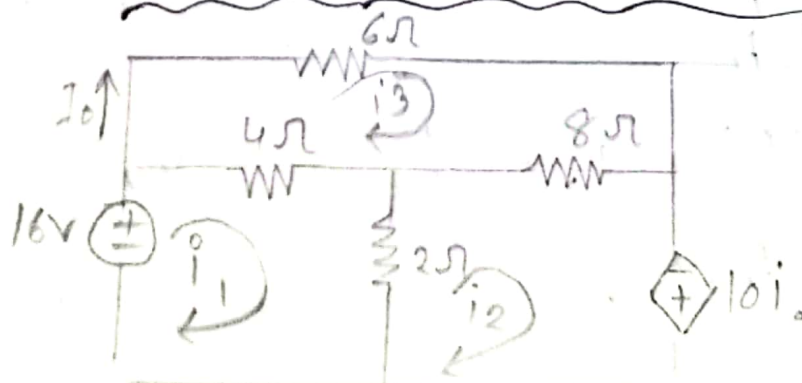

Solution: Apply KVL to mesh-1:

$$-16 + 6i_1 - 2i_2 - 4i_3 = 0$$
$$\Rightarrow 3i_1 - i_2 - 2i_3 = 8 \quad \text{--- (1)}$$

Mesh-2: $-10i_0 - 2i_1 + 10i_2 - 8i_3 = 0$

$$\Rightarrow -2i_1 + 10i_2 - 18i_3 = 0 \quad [i_0 = i_3]$$
$$\Rightarrow -i_1 + 5i_2 - 9i_3 = 0 \quad \text{--- (2)}$$

Mesh-3: $18i_3 - 4i_1 - 8i_2 = 0 \quad \text{--- (3)}$

Using Cramer's rule:

$$\begin{bmatrix} 3 & -1 & -2 \\ -1 & 5 & -9 \\ -2 & -4 & 9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 8 \\ 0 \\ 0 \end{bmatrix}$$

$$\therefore i_1 = \frac{-18}{7} = -2.57 \text{ A}$$


$$\therefore i_2 = \frac{-54}{7} = -7.71 \text{ A}$$

$$\therefore i_3 = -4 \text{ A}$$

we know, $i_0 = i_3 = -4 \text{ A}$

Ans: $i_0 = -4 \text{ A}$

Ans. to the Q. NO :05

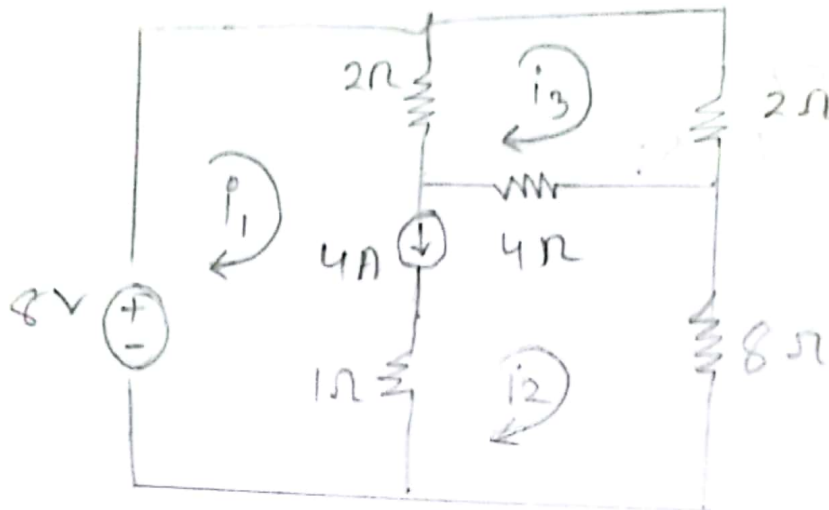

Solution: Apply KVL to mesh-1:

$$-8 + 2i_1 - 2i_3 + 4 = 0$$

$$\Rightarrow 2i_1 - 2i_3 = 4$$

$$\Rightarrow i_1 - i_3 = 2 \quad \text{--- (1)}$$

Mesh-2: $8i_3 - 4i_2 - 4 = 0$

$$\Rightarrow -i_2 + 2i_3 = 1 \quad \text{--- (2)}$$

Mesh-3: $-2i_1 - 4i_2 + 8i_3 = 0$

$$\Rightarrow -i_1 - 2i_2 + 4i_3 = 0 \quad \text{--- (3)}$$

using Cramer's rule :

$$\begin{bmatrix} 1 & 0 & -1 \\ 0 & -1 & +2 \\ -1 & -2 & +4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 1 \\ 0 \end{bmatrix}$$

$$\therefore i_1 = 2A$$

$$\therefore i_2 = -1A$$

$$\therefore i_3 = 0A$$

Ans: