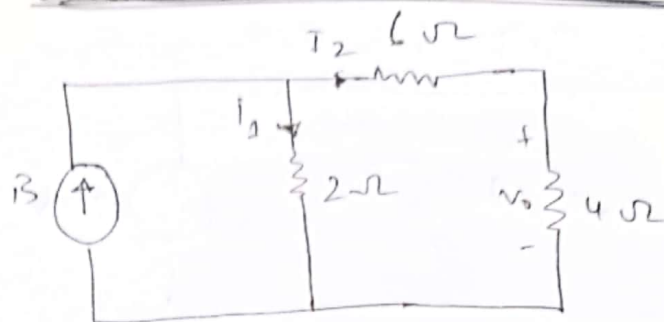


Ahmed Al-khatir

ID: 170103020038

Assignment - 02 D: 25/01/20

4.1




$$\text{division, } i_2 = \frac{2}{2+6+4} i_s = \frac{1}{6} i_s$$

$$v_0 = 4i_2 = \frac{2}{3} i_s$$

$$\therefore i_s = 15 \text{ A}, v_0 = \frac{2}{3} (15) = 10 \text{ V}$$

$$\therefore i_s = 30 \text{ A}, v_0 = \frac{2}{3} (30) = 20 \text{ V}$$

4.2

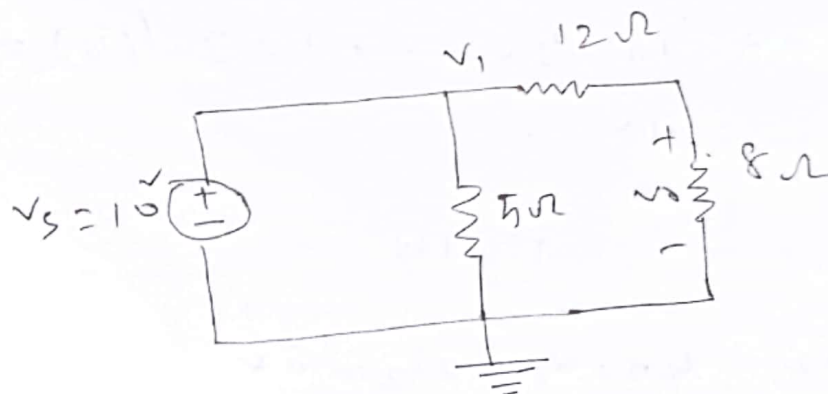

$$\text{Let, } v_0 = 1$$


$$i = \frac{1}{8}$$

$$v_1 = \frac{1}{8} (12+8) = 2.5$$


$$\therefore v_s = 2.5 \text{ V}$$

$$v_s = 10 \text{ V, then } v_0 = 4 \text{ V}$$

4.3

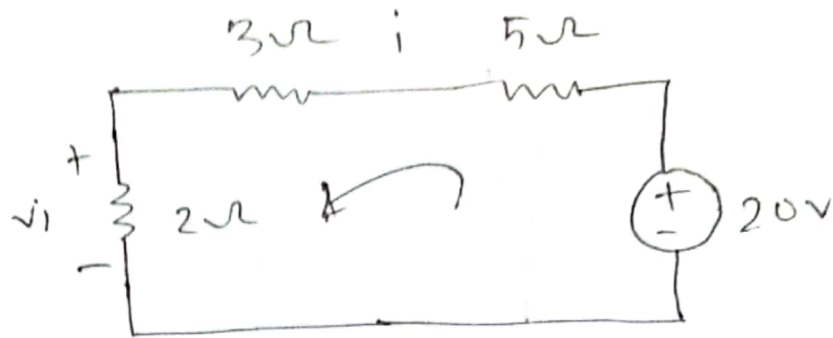

(a)

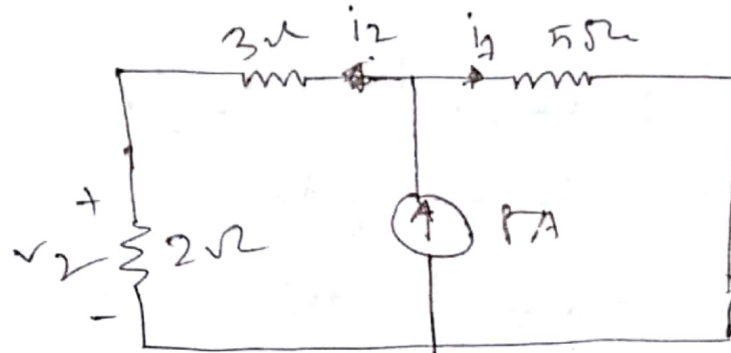

(b)

Get, v_1 — — — Fig (a)

$$(2 + 3 + 5) i = 20 \rightarrow i = 20 / (10) = 2A$$



$$v_1 = 2i = 4V$$

Get v_2 — — — Fig (b)

$$i_1 = i_2 = 4A, v_2 = 2i_2 = 8V$$

$$\therefore v = v_1 + v_2 = 4 + 4 = 12V$$

4.4

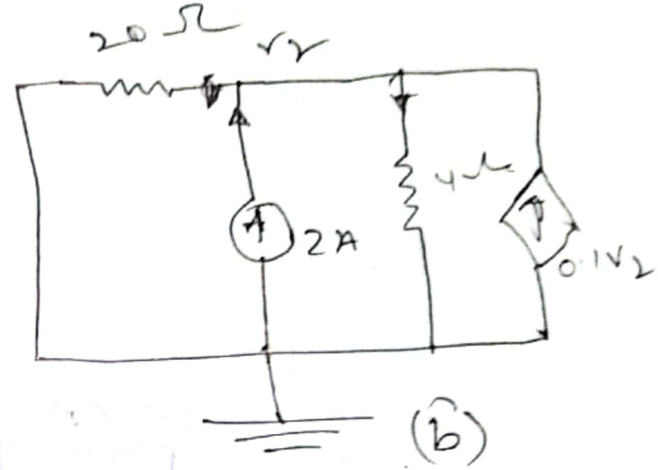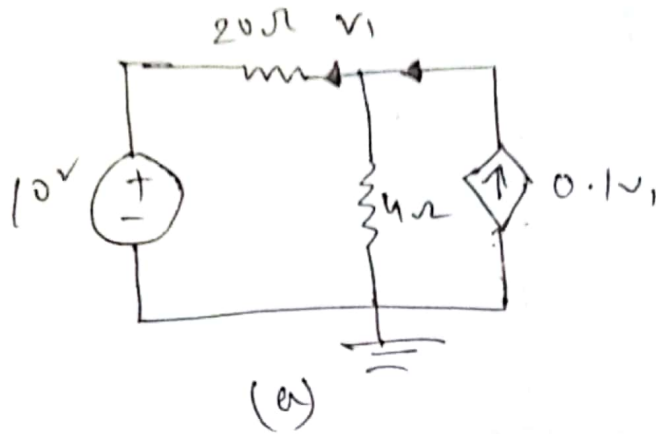

Let, v_1 consider Fig (a)



$$0.1v_1 + \frac{10 - v_1}{20} = \frac{v_1}{4} \rightarrow v_1 = 2.5$$

$\therefore v_2$ consider Fig (b).

$$2 + 0.1v_2 + \frac{0 - v_2}{20} = \frac{v_2}{4} \rightarrow v_2 = 10$$

$$\therefore v_x = v_1 + v_2 = 12.5 \checkmark$$

4.7

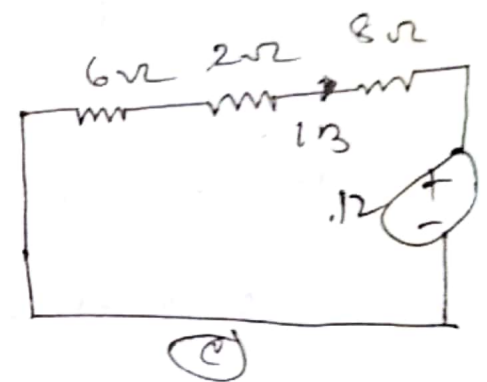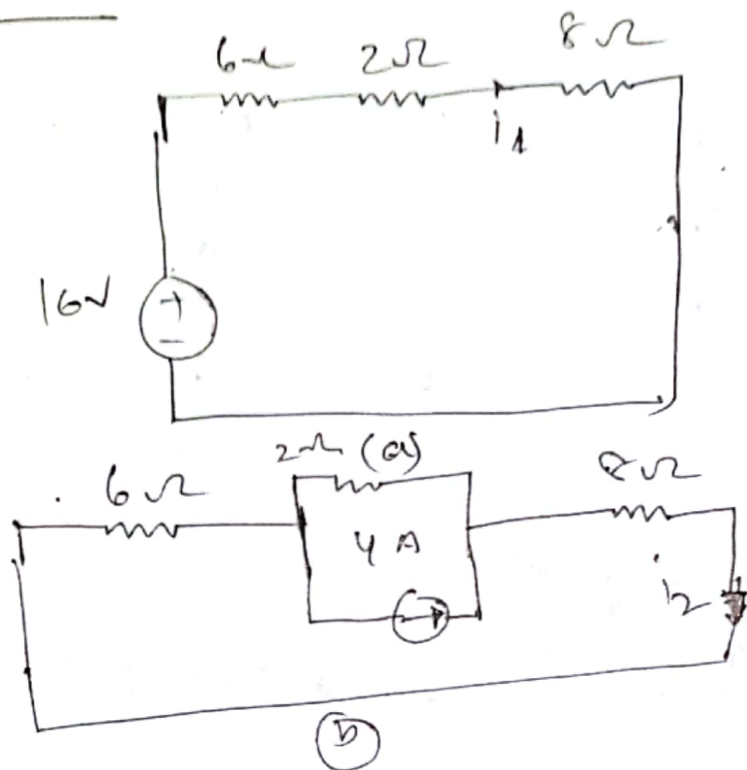

For i_1 , consider Fig (a)

$$i_1 = \frac{16}{6+2+8} = 1 \text{ A}$$

\therefore For i_2 consider Fig (b)




$$i_2 = \frac{2}{2+14} \text{ (A)} = 0.5$$

\therefore For i_3 consider Fig (c)

$$i_3 = \frac{-12}{16} = -0.75 \text{ A}$$

$$\begin{aligned} \text{Thus, } i &= i_1 + i_2 + i_3 \\ &= 1 + 0.5 - 0.75 \\ &= \underline{750 \text{ mA}} \end{aligned}$$

u.6.

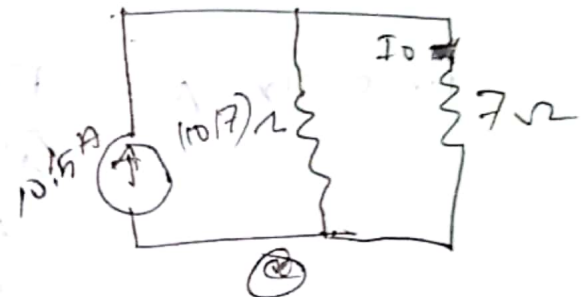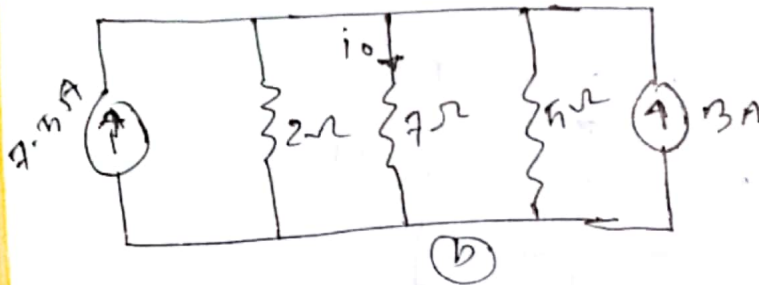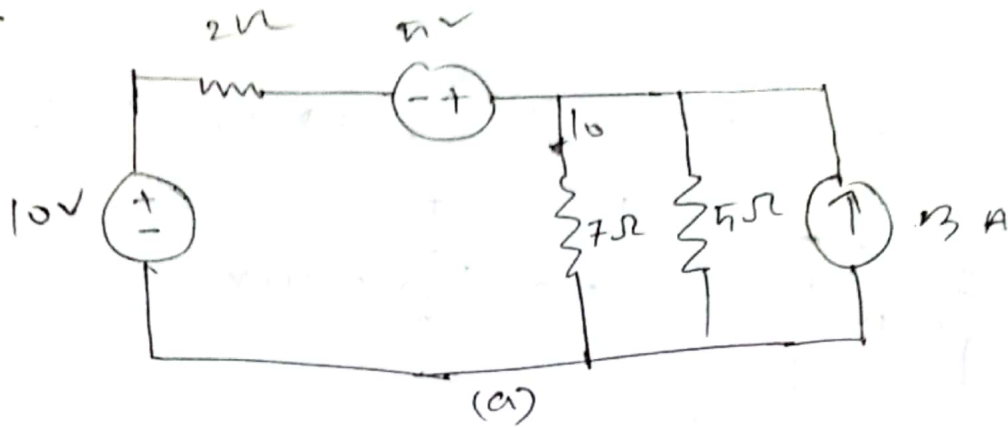


Adding the 10V and 15V voltage source 15V voltage. transform the 15V + source in series 2-Ω resistor eqv. circuit (b) combine the two current sources 2-Ω 15-Ω resistor leads to the circuit in Fig (c) using circuit division.

$$i_o = \frac{\frac{10}{7}}{\frac{10}{7} + 7} \quad (10.7)$$


$$= \underline{1.78A}$$

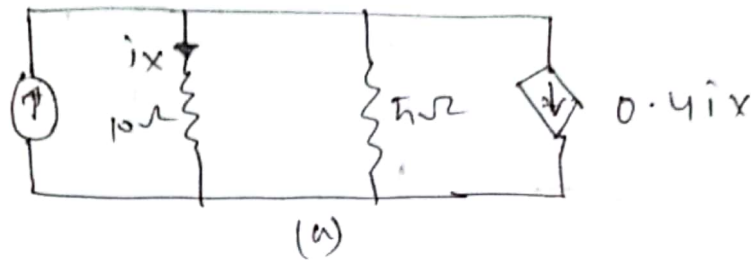4.7

$$i_x = \frac{5}{15} (4 - 0.4i_x) \rightarrow i_x = 1.76 \text{ A}$$





$4 - 0.4i_x$ A

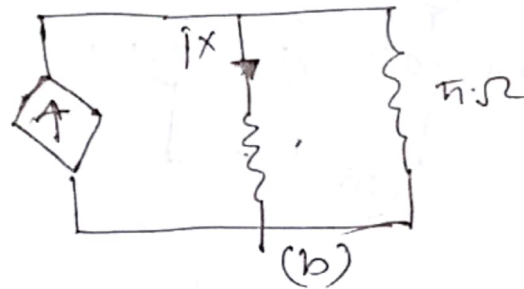

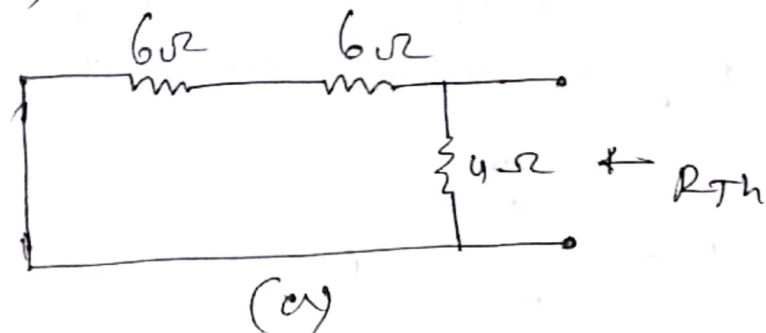4.8


To find R_{th} , consider the circuit in Fig. (a)



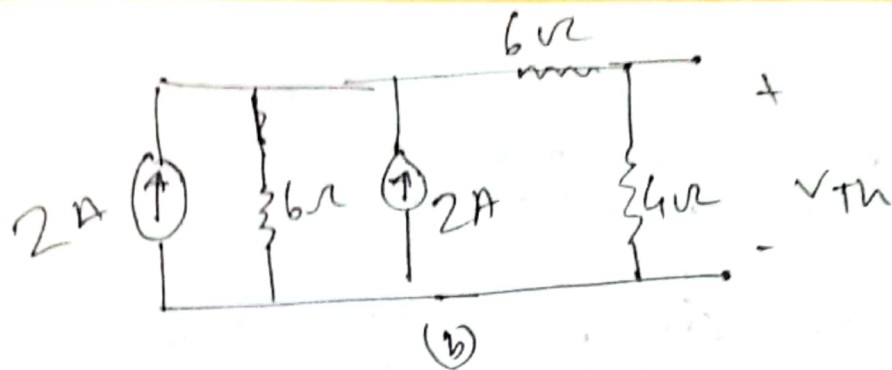

$$R_{th} = (6+6) \parallel 4 = \frac{12 \times 4}{18} = 3\Omega$$

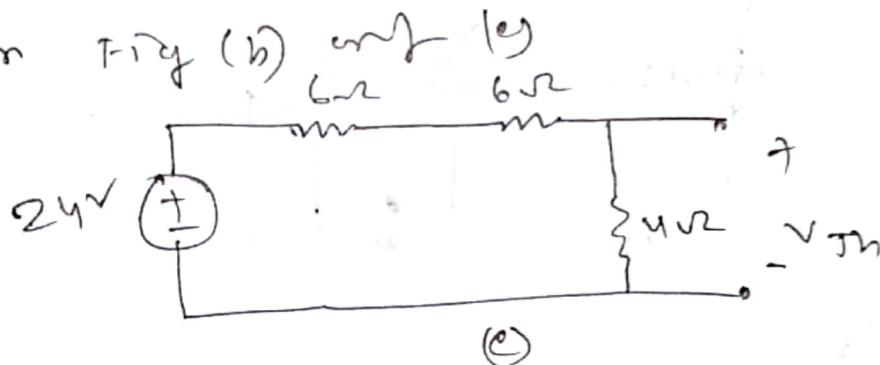To find V_{th} , we use source transformation



using div in Fig (c)

$$V_{th} = \frac{4}{4+12} (24) = 6V$$



$$i = \frac{V_{th}}{R_{th} + 1}$$

$$= \frac{6}{3+1}$$

$$= 1.5 A$$

4.9

To find V_{Th} consider circuit Fig (a)

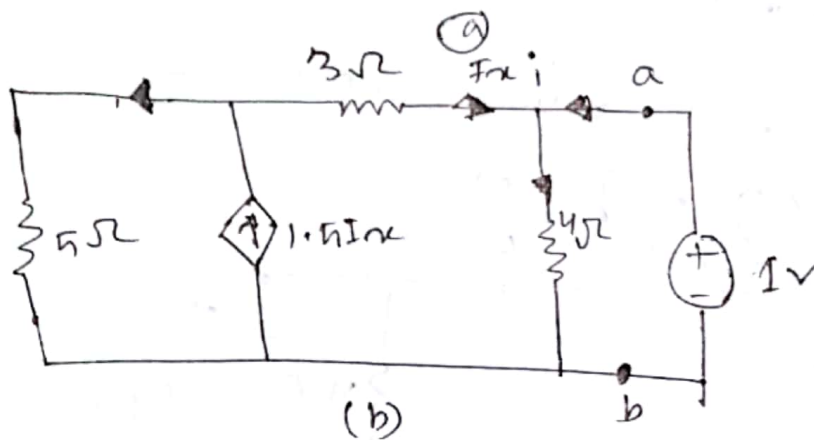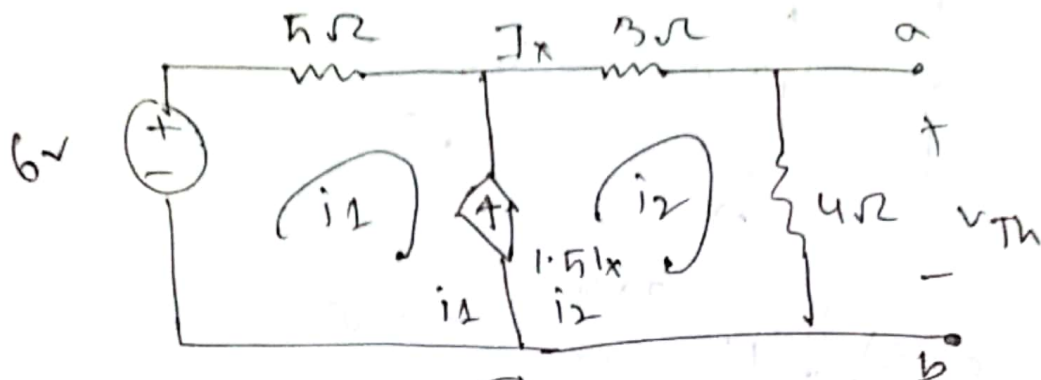

$$I_x = i_2$$

$$i_2 - i_1 = 1.5 I_x = 1.5 i_2 \rightarrow i_2 = -2 i_1 \quad \text{--- (1)}$$

$$\text{For the mesh } -6 + 5i_1 + 7i_2 = 0 \quad \text{--- (2)}$$

$$\text{From (1) and (2), } i_2 = 4/13 \text{ A}$$

$$V_{Th} = 4i_2 = 5.333 \text{ V}$$

To find R_{Th} consider Fig (b) applying KVL around the outer loop.



$$5(0.5I_x) - 1 - 1 - 3I_x = 0 \rightarrow I_x = -2$$

$$i_2 = \frac{1}{4} - I_x = 2.25$$

$$R_{Th} = \frac{4}{1} = \frac{1}{2.25} = 444.4 \text{ m}\Omega$$

4.10 since there are no independent sources

$$V_{th} = 0$$

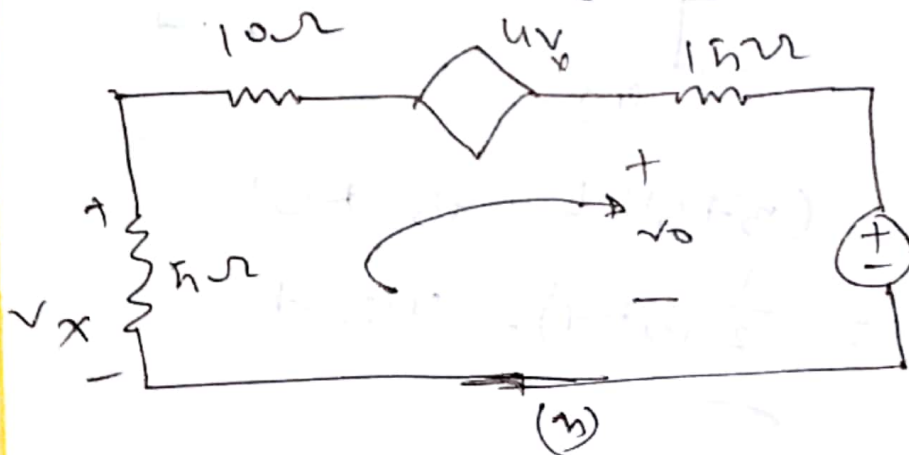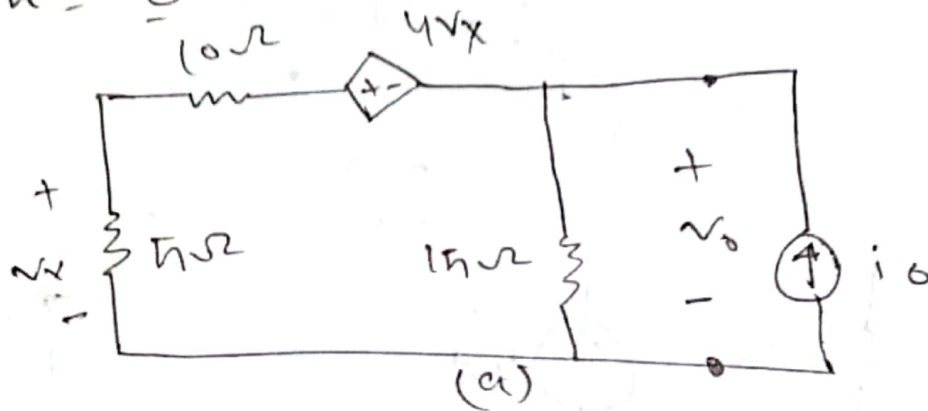

To find R_{th} consider Fig (a) using source transfer the circuit is transfer to that in Fig (b) applying KVL

$$\text{But } V_x = 5i, \text{ Hence, } 30i - 20i + 15i_0 = 0 \rightarrow 10i = -15i_0$$

$$V_0 = (15i + 15i_0) = 15(-15i_0 + i_0) = -7.5i_0$$

$$R_{th} = V_0 / (i_0) = -7.5\Omega$$

4.11


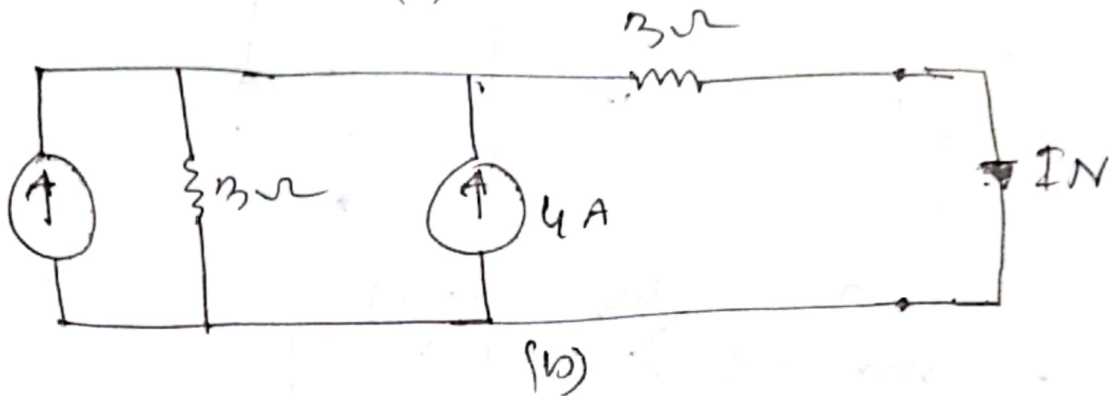
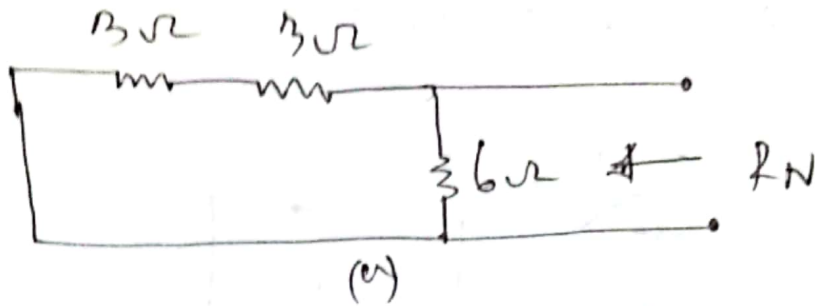
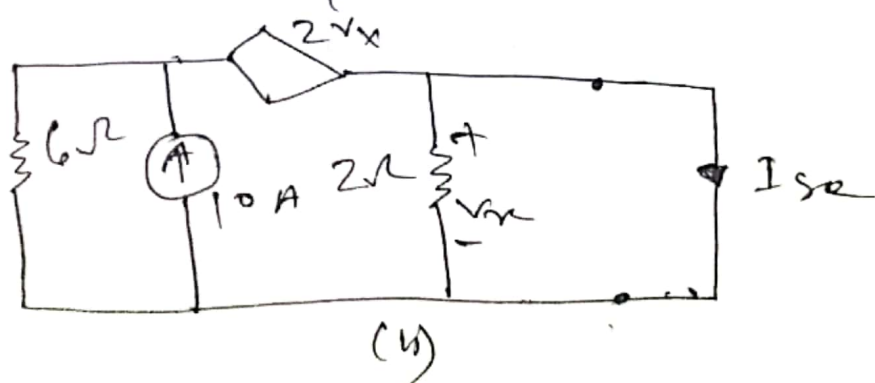


Fig (a) $R_N = (3+3) \parallel 6 = 3\Omega$

Fig (b) $I_N = \frac{1}{2}(5+4) = 4.5A$

4.12

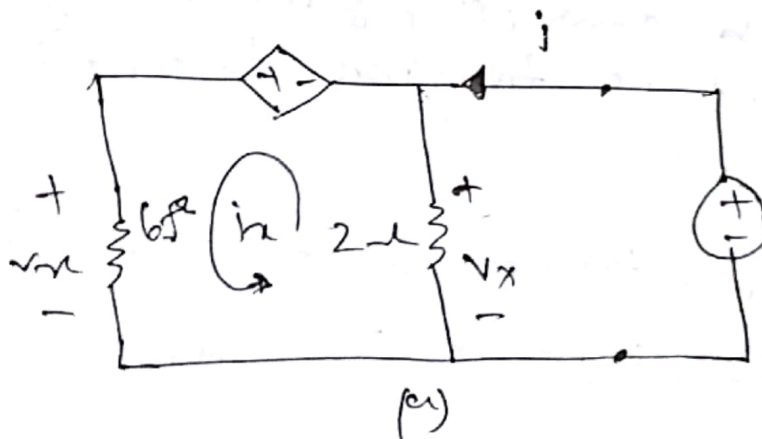

To get R_N consider the circuit fig (a)

Applying KVL, $6i_N - 2v_N - 1 = 0$



But $v_N = 1$, $6i_N = 3 \rightarrow i_N = 0.5$

$$i = i_N + \frac{v_N}{2} = 0.5 + 0.5 = 1$$

$$R_N = R_{Th} = \frac{1}{i} = 1 \Omega$$

To find I_N consider circuit in fig (b)
 Because 2Ω resistor is shorted, $v_N = 0$ and
 the dependent source is inactive
 Hence $I_N = i_{sc} = 10 A$

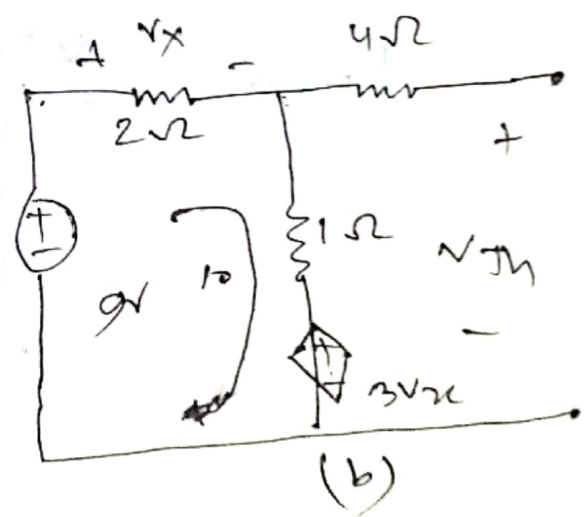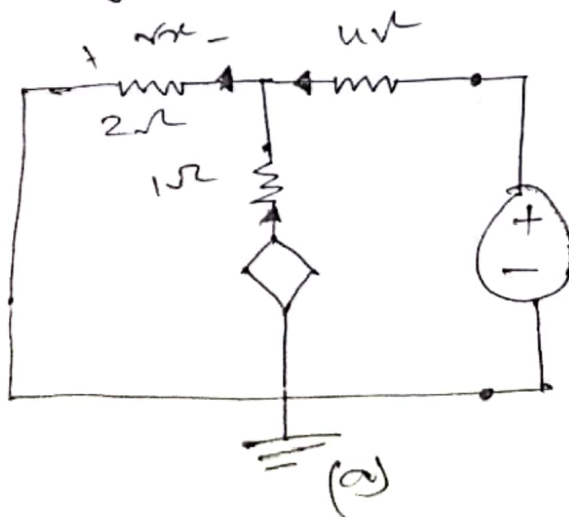4.13 we first find R_{Th} and V_{Th} .
 to find R_{Th} we consider the circuit
 in fig (a)



Applying KCL at the top node gives

$$\frac{1-v_0}{4} + \frac{3v_x - v_0}{1} = \frac{v_0}{2}$$

But $v_x = -v_0$. Hence

$$\frac{1-v_0}{4} - 4v_0 = \frac{v_0}{2} \rightarrow v_0 = 1/19$$

$$1 = \frac{1-v_0}{4} = \frac{1 - \frac{1}{19}}{4} = \frac{9}{38}$$

$$R_{TH} = 1/\frac{9}{38} = 38/9 = 4.222 \Omega$$

To find v_{TH} consider circuit fig (b)

$$-9 + 2i_0 + i_0 + 3v_x = 0$$

But $v_x = 2i_0$, Hence

$$9 = 3i_0 + 6i_0 = 9i_0 \rightarrow i_0 = 1 \text{ A}$$

$$v_{TH} = 9 - 2i_0 = 7 \text{ V}$$

$$R_1 = R_{TH} = 4.222 \Omega$$

$$P_{max} = \frac{v_{TH}^2}{4R_L}$$

$$= \frac{49}{4(4.222)}$$

$$= 2.901 \text{ W}$$